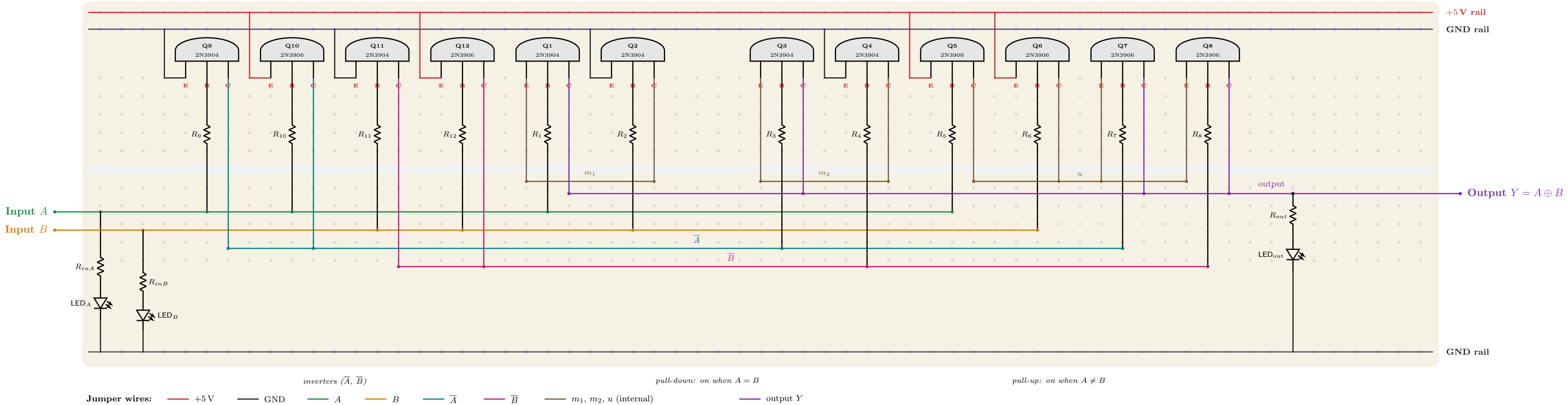




Each column of five holes in a bank is one node; transistor legs are *EBC* in **adjacent** holes.

One standard full-size (830-point) breadboard. The two GND rails are **one node** – bridge them with a jumper at the board edge.